

ELEC 2501 Mid Term #1, Oct. 17th, 2020

Instructions (READ!!!!!!)

- 1) The exam will last 1.5 hours.
- 2) This is a closed book exam.
- 3) Show all work.
- 4) Your solutions to all problems must fit on six one sided 8 ½ X 11 sheets of paper or less.
- 5) Place a large and very obvious BOX around your final answer for each question.
- 6) Solutions MUST be uploaded within 15 mins after the exam ends to be counted.
- 7) There are eight questions. Each is worth equal marks.

Formulas that might be useful:

$$\omega = 2\pi f, T = \frac{1}{f}, \sqrt{\frac{1}{T_2 - T_1} \int_{T_1}^{T_2} (f(t))^2 dt}, i(t) = \frac{dq(t)}{dt}, v = \frac{dw}{dq}, p(t) = v(t) \cdot i(t), v = iR,$$

$$\sum_{j=1}^N i_j(t) = 0, \sum_{j=1}^N v_j(t) = 0, \frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}, R_S = R_1 + R_2 + \dots + R_N$$

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3} R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3} R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b} R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$C = \frac{\epsilon \cdot A}{d}, i = C \frac{dv}{dt}, E(t) = \frac{1}{2} C v^2(t), \frac{1}{C_S} = \sum_{i=1}^N \frac{1}{C_i} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}, C_P = \sum_{i=1}^N C_i$$

$$v(t) = L \frac{di(t)}{dt}, E(t) = \frac{1}{2} L i^2(t), L_S = \sum_{i=1}^N L_i, \frac{1}{L_P} = \sum_{i=1}^N \frac{1}{L_i} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$

$$x(t) = K_1 + K_2 e^{-\frac{t}{\tau}}, \tau = RC, \tau = \frac{L}{R}$$

$$Z = R, Z = j\omega L, Z = \frac{1}{j\omega C}, Z_S = Z_1 + Z_2 + \dots + Z_N, \frac{1}{Z_P} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}, Y = \frac{1}{Z}$$

$$Y_P = Y_1 + Y_2 + \dots + Y_N, \frac{1}{Y_S} = \frac{1}{Y_1} + \frac{1}{Y_2} + \dots + \frac{1}{Y_N}$$


$$\omega_o = \frac{1}{\sqrt{LC}}, Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o CR} = \frac{1}{R} \sqrt{\frac{L}{C}}, \omega_{LO} = \omega_o \left[\frac{-1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right], \omega_{HI} = \omega_o \left[\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

$$BW = \omega_{HI} - \omega_{LO} = \frac{\omega_o}{Q}, \omega_{HI} \cdot \omega_{LO} = \omega_o^2, Q = 2\pi \frac{\omega_S}{\omega_D}, \omega_r = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}$$

$$P = \frac{V_{MIM}}{2} \cos(\theta_v - \theta_i) = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i), PF = \cos(\theta_v - \theta_i) = \cos(\theta_{Z_L}) = \cos(-\theta_{Z_L}),$$

$$S = V_{RMS} I_{RMS}^*, \frac{i_1}{i_2} = \frac{v_2}{v_1} = \frac{N_2}{N_1}, Z_p = \left(\frac{N_p}{N_s}\right)^2 Z_s$$

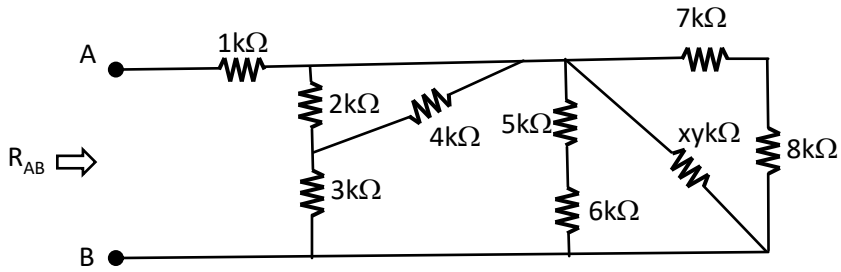
1) Find the resistance R_{AB} of the following circuit:




Note that xy are the last two digits of your student number.

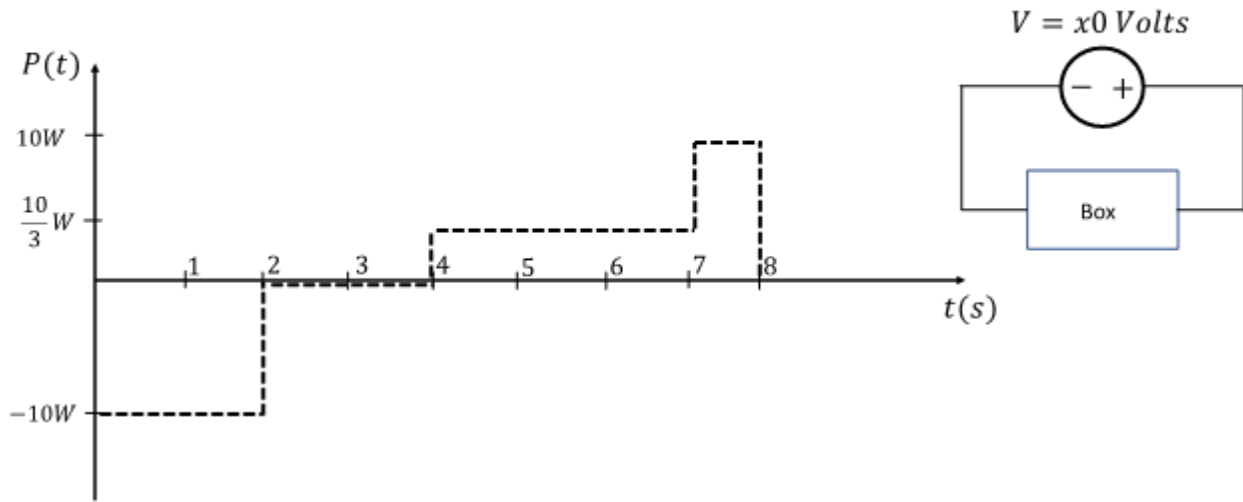2)


The power absorbed by the box is shown below. The voltage supplied by the source is $V = x0V$, where x is the last digit of your student number. If your student number ends in 1 then $V = 10V$ etc. If your student number ends in zero then $V = 100V$. Find the total charge entering the box between 2 and 8 seconds.



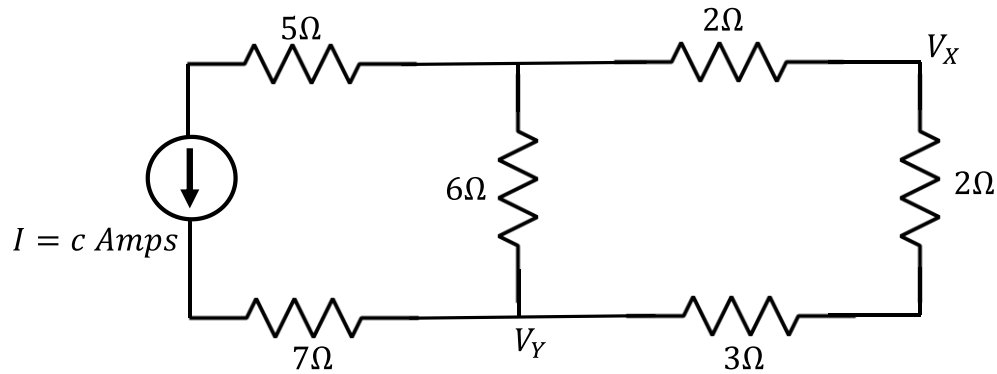- 3) Calculate $V_{YX} = V_Y - V_X$ in the circuit shown. Here, 'c' is the last digit of your student number ex. Student number ends in a 2 so $I = 2A$. If your student number ends with 0 then $I = 10A$.




- 4) For the following circuit:

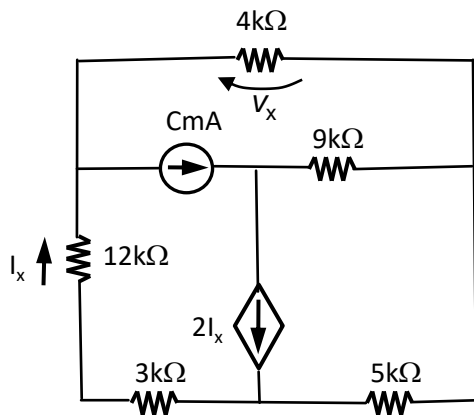


Find V_x . Note that C is the last digit of your student number. If the last digit of your student number is zero, $C = 10mA$.

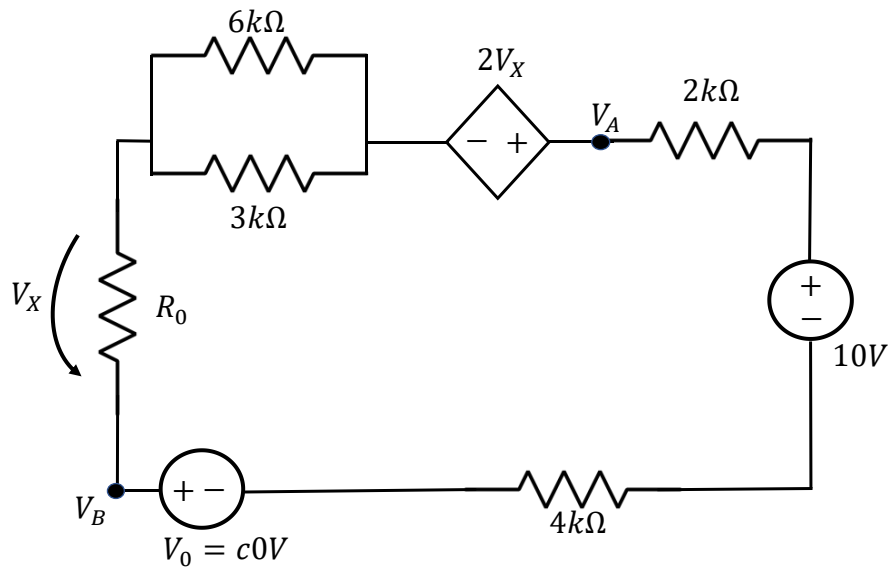- 5) Given that the source V_0 **absorbs** 100mW of power, find $V_{BA} = V_B - V_A$. Here, 'c' is the last digit of your student number. So, if the last digit of your student number is 3 then the voltage source is $V_0 = 30V$. If your student number ends in zero, then $V_0 = 100V$.




- 6) For the following circuit:

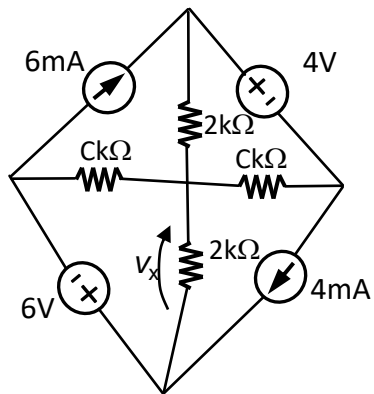

Find V_x . Note that C is the last digit of your student number. If the last digit of your student number is zero, $C = 10k\Omega$.

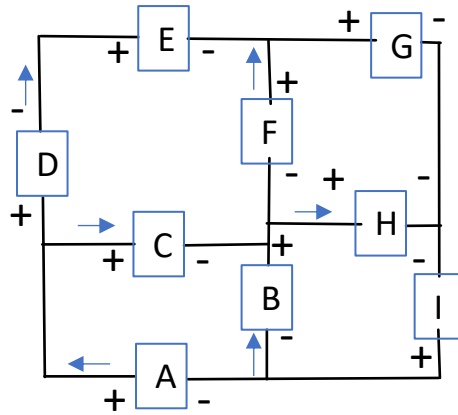- 7) In the following circuit some measured voltages and currents are labeled. Which elements in the circuit CANNOT be resistors?



- 8) For the following circuit find the resistance between point x and y, note that A is the last digit of your student number.

