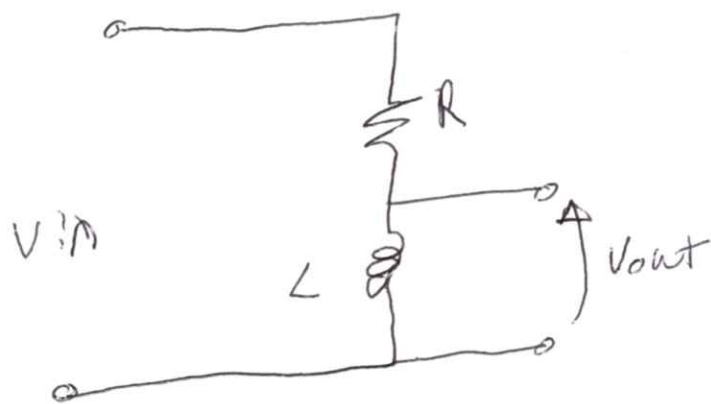


2501 Final 2020 Sols

①



~~$\tau = \frac{L}{R}$~~

$$\tau = \frac{L}{R}$$

$$\frac{V_{out}}{V_{in}} = \frac{j\omega L}{R + j\omega L}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \frac{9}{18} = \frac{1}{2}$$

$$\frac{\omega^2 L^2}{R^2 + \omega^2 L^2} = \frac{1}{4}$$

$$4\omega^2 L^2 = R^2 + \omega^2 L^2$$


$$3\omega^2 L^2 = R^2$$

$$\tau^2 = \frac{L^2}{R^2} = \frac{1}{3\omega^2}$$

$$\tau = \frac{1}{\sqrt{3}\omega}$$

$$\tau = \frac{1}{\sqrt{3}(2\pi \cdot 1 \times y \times 10^3)}$$
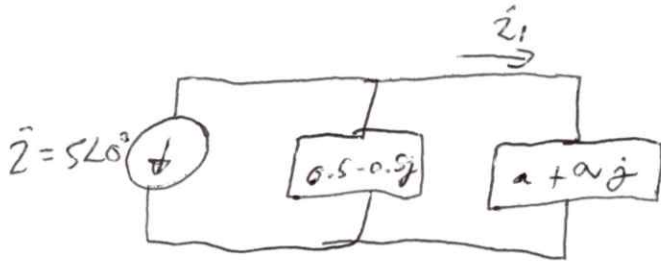
$$\textcircled{2} \quad (1\Omega // -j) = 0.5 - 0.5j \quad \text{let } a = \gamma + 1$$



$$\bar{z}_1 = \bar{z} \left(\frac{0.5 - 0.5j}{0.5 - 0.5j + a + aj} \right) \quad (\text{current divider})$$

$$\text{Power in Resistor} = \frac{|\bar{z}_1|^2}{2} \quad (a)$$


③ let $s = j\omega$

$$G_v(s) = \frac{(10\alpha + s)}{(s + s - s_j)(s + s + s_j)(\frac{s}{1000} + 1)}$$



$$\begin{aligned} & \frac{(s + s - s_j)(s + s + s_j)}{= s^2 + s s + s_j s + s s - s_j s + (s - s_j)(s + s_j)} \\ & = s^2 + 10s + 50 \end{aligned}$$

$$G(\omega) = \frac{10\alpha \left(\frac{s}{10\alpha} + 1\right)}{(s^2 + 10s + 50) \left(\frac{s}{1000} + 1\right)} = \frac{\frac{\alpha}{s} \left(\frac{s}{10\alpha} + 1\right)}{\left(\frac{s^2}{50} + \frac{s}{5} + 1\right) \left(\frac{s}{1000} + 1\right)}$$


$$\sqrt{50} \approx 7.1$$

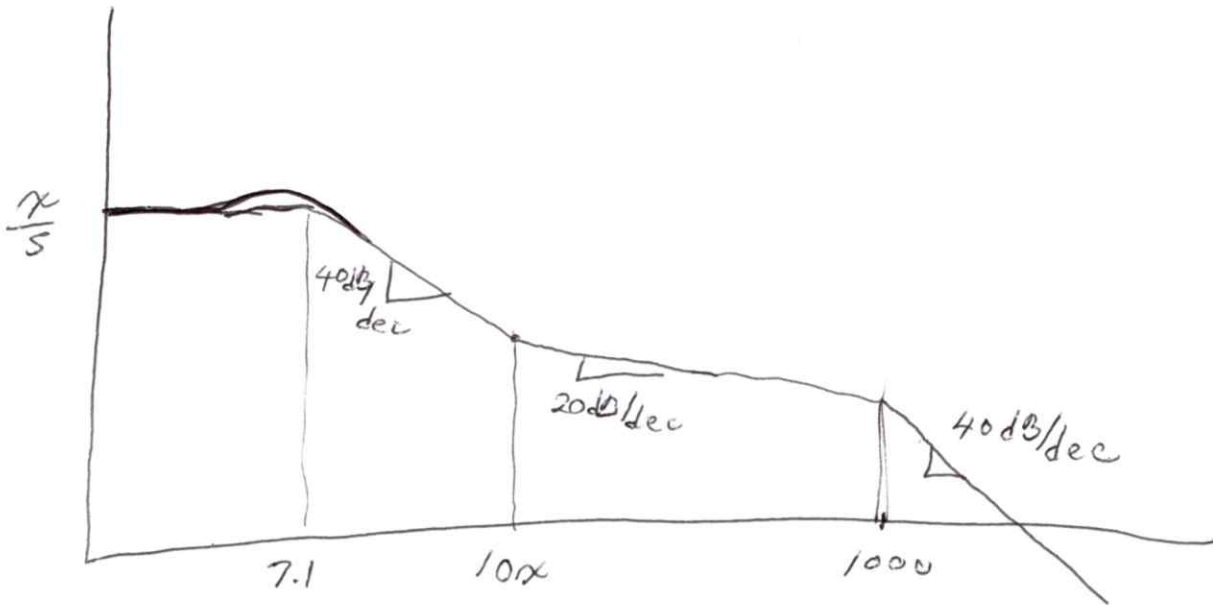

④ Left side let $a = \gamma + 1$

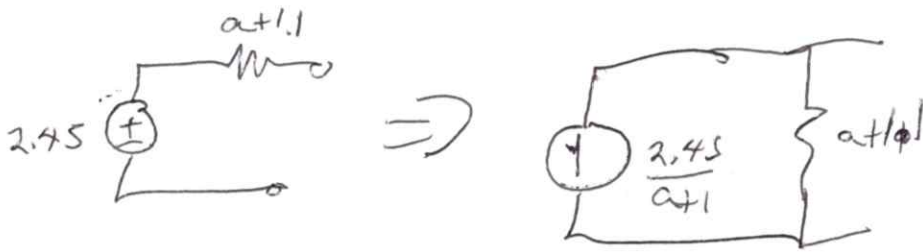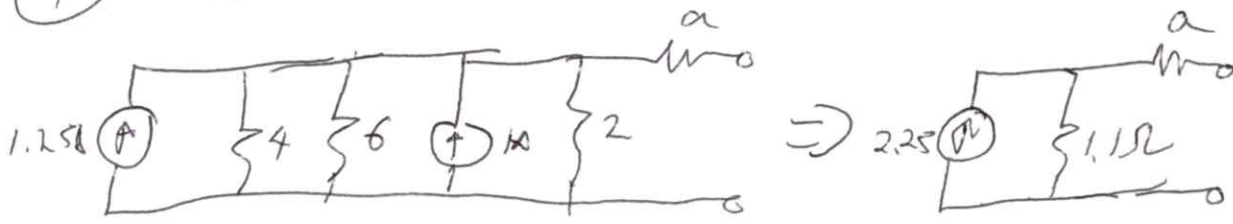


right side let $b = \gamma + 1$

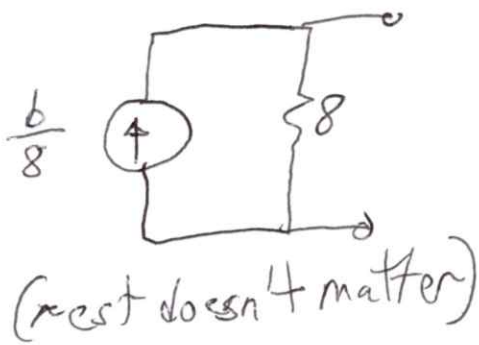

total Norton

$$\frac{b}{8} + \frac{2.45}{a+1}$$

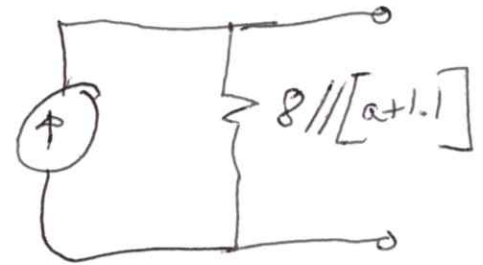

5


$$v_{L0} = v_0 \left[\frac{-1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

$$v_{L0} = v_0 \left[-0.00625 + 1 \right]$$

$$\cancel{v_{L0}} \rightarrow v_0 = \frac{v_{L0}}{0.994} = \frac{8000}{0.994} = 8048.3$$

output will be zero
at this freq.
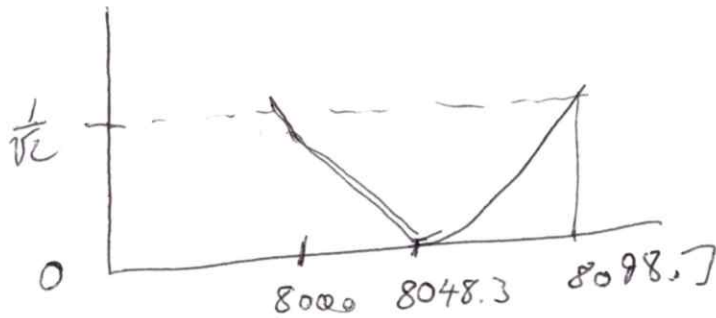
$$v_H = v_0 \left[\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 8048.3 (1.0063) \\ = 8098.7$$



⑥

$$R_{th} = 13 \Omega$$

$$V_{th} = 7(2+y)$$

$$\therefore R_{Load} = 13 \Omega$$

$$V_{Load} = \frac{V_{th}}{2} \quad \therefore P_{Load} = \frac{\left(\frac{V_{th}}{2}\right)^2}{13}$$

⑦ ϵ initial current from supply

$$I = \frac{(3+1)}{1M + 2M \parallel 2M} = \frac{y+1}{2000}$$

$$I_{\text{hint}} = -\frac{y+1}{4000} \quad \begin{array}{l} \text{(half supply current)} \\ \text{(flows right to left)} \end{array}$$

$$I_{\text{final}} = \frac{y+1}{2000} \quad \text{(flows left to right)}$$

resistance seen by L: $R_{\text{eq}} = 2M \parallel 1M = 667 \Omega$

$$\tau = \frac{L}{R} = \frac{1}{667} = 1.5 \text{ms}$$

$$i(t) = k_1 + k_2 e^{-\frac{(t-1\text{ms})}{\tau}}$$

$$i(1\text{ms}) = k_1 + k_2 = -\frac{y+1}{4000}$$


$$i(\infty) = k_1 = \frac{y+1}{2000}$$

$$k_2 = -\frac{y+1}{4000} - \frac{y+1}{2000} = -\frac{3(y+1)}{4000}$$


$$i(t) = \frac{(y+1)}{2000} + \frac{3(y+1)}{4000} e^{-\frac{(t-1\text{ms})}{\tau}}$$

$$V_x(t) = L \frac{di}{dt} = 3L \left(\frac{y+1}{4000} \right) e^{-\frac{(t-1\text{ms})}{\tau}} \cdot \frac{1}{\tau}$$
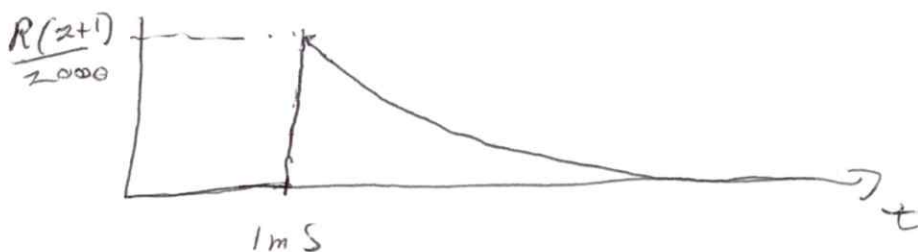
$$= 3R \left(\frac{y+1}{4000} \right) e^{-\frac{(t-1\text{ms})}{\tau}}$$



8) move everything to the primary

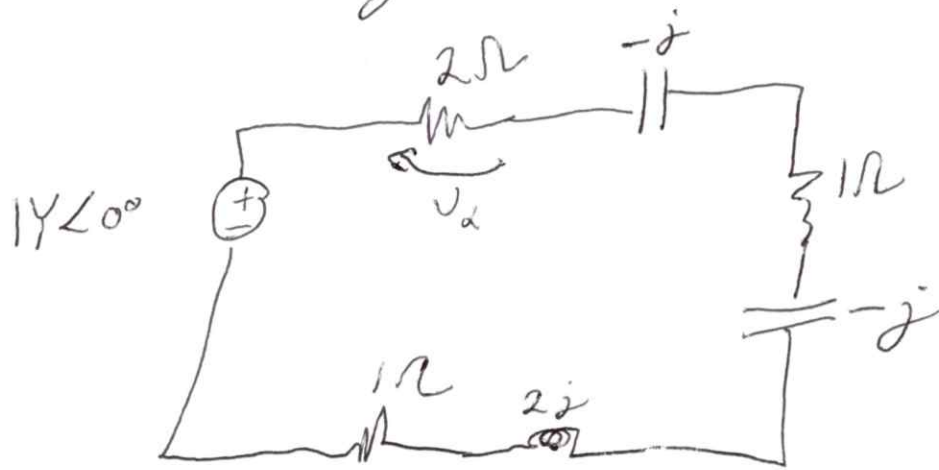

$$V_x = \frac{1V}{2} \angle 0^\circ$$