

97.455 Exam Solutions for 2001

Note: 97.455 2001 Final Exam Questions have been corrected so make sure you download the latest version on my web page

Question 1 $Y_{in} = 0.1m + j1m$, $BW = 100\text{kHz}$, $f_o = 1\text{ MHz}$.

- $R=10\text{ k}\Omega$ and $C=159.155\text{pF}$.
- $\frac{N_1}{N_2} = 0.0707$, $R_{TOT} = 5k$, $C_{TOT} = 318.310\text{ pF}$, $C_{ADD} = 159.155\text{ pF}$, $L = 79.577\mu\text{H}$.
- If $Q_L = 100$, $R_p = \omega L \times 100 = 50k$, center frequency remains the same but bandwidth increases to 110 KHz (10%).
- $L=112.26\ \mu\text{H}$ and $C=65.36\text{ pF}$.

Question 2

- Filter 1 $BW \geq 19.8\text{ MHz}$, f_0 at 98.1 MHz
 - Filter 2 $BW \simeq 0.2\text{ MHz}$, f_0 at 10.7 MHz
 - $f_{LO} = f_{RF} + 10.7\text{ MHz}$, nominal 108.8 MHz.
- Image frequency is $f_{RF} + 2f_{IF} = 119.5\text{ MHz}$, Any signal or noise at this frequency will also mixed down to our frequency of interest. The image reject filter removes it.
- Adjacent channels are also mixed down tot the 10.7 MHz region e.g. 89.9 - 10.0 and 98.3 to 10.5 MHz. IF filter removes these.
- Intermodulation by any two frequencies with Δf between them where one is Δf away from the RF signal. e.g. At Δf and $2\Delta f$ away e.g. 98.3 and 98.5 MHz, remove by making circuit linear.

Question 3

- RF input need to be more linear than the LO input to avoid intermodulation of multiple RF inputs. LO is a known frequency and harmonics can help switching. High linearity can be achieved by degeneration resistance in series with emitters as shown in class. Linearity estimated from $V_{max} = i_{bias} \cdot (R_E + r_e)$.
- Two signals added amplitude A,B. $A=4$ and $B=1$, $f_A = 2\text{ MHz}$ and $f_{mod} = 50\text{ kHz}$. separated by $2f_{mod}$ e.g. signals are $f_c \pm 2f_{mod}$ where f_c is suppressed. so 2 MHz and 2.1 MHz or 1.90 MHz and 2 MHz.

Question 4 Conducts for $10\ \mu\text{s}$, off for $40\ \mu\text{s}$, $I_{peak} = 10\text{ mA}$, $V_{CC} = 10\text{ V}$, $n=2$.

a) $\Theta = \frac{\pi}{5} = 36^\circ$, $T = 50 \mu s$, input frequency is 40 kHz.

b) $I_p = 52.36 \text{ mA}$, $I_{DC} = 1.3244 \text{ mA}$, $P_{DC} = 13.244 \text{ mW}$, $I_2 = 2.2564 \text{ mA}$, $P_{2,max} = 11.2821 \text{ mW}$.

c) $\eta_{max} = \frac{P_2}{P_{DC}} = 85.19\%$

Question 5 PLL for LO generation for FM receiver

Need $f_{RF} + f_{IF}$ or $(88.1 - 107.9 \text{ MHz}) + 10.7 \text{ MHz}$ in steps of 200 kHz or 98.8 - 118.6 MHz in steps of 200 kHz.

a) Block Diagram (Done in class)

b) Choose $\xi = 0.707$, then settling time is $\omega_n t \approx 4.5$

$$\omega_n = \frac{4.5}{t} = \frac{4.5}{1m} = 4500 \text{ rad/sec}$$

c) Channel at 98.1 has $f_{LO} = 108.8$, or $N=544$ switching to $N=545$ for 200 kHz step of 200 kHz/545 = 366.97 Hz or 2305.76 rad/sec. Phase error from graph is peak at:

$$\frac{\epsilon}{\frac{\Delta\omega}{\omega_n}} = 0.46 \text{ or}$$

$$\epsilon = 0.46 \times \frac{\Delta\omega}{\omega_n} = 0.46 \times \frac{2305.76}{4500} = 0.2357 \text{ rad}$$

Will lose lock if $\epsilon = 2 \cdot \pi$ for three state detector.

$$\Delta\omega = \frac{\epsilon\omega_n}{0.46} = \frac{2\pi \times 4500}{0.46} = 61465.9 \text{ rad/sec} = 2\pi \times 9782.6 \text{ Hz}$$

At output 544 times higher on $2\pi \times 5.32 \text{ MHz}$.

d) $\omega_n = \sqrt{\frac{K}{N\tau_1}}$ or $\tau_1 = \frac{K}{\omega_n^2 N} = \frac{0.4 \times 2\pi \times 10M}{4500^2 \cdot 545} = 2.277 \text{ ms}$

$$\xi = \frac{\omega_n \tau_2}{2} \text{ or } \tau_2 = \frac{2\xi}{\omega_n} = \frac{2 \times 0.707}{4500} = 314.2 \mu s$$

e) Plot and explanation already done in class

Question 6

$N_{o,add} = 0.5N_{o,src}$ given.

$$F = \frac{N_{o,tot}}{N_{o,src}} = \frac{N_{o,src} + N_{o,add}}{N_{o,src}} = \frac{N_{o,src} + 0.5 \cdot N_{o,src}}{N_{o,src}} = 1.5$$

$$NF = 10 \cdot \log_{10}(1.5) = 1.76 \text{ dB.}$$

Question 7

a) Open Loop gain larger than 1 at 0° point.

- Moves C.L. poles into RHP which guarantees startup and oscillation with finite (nonzero) amplitude.
- Aiming for exactly gain of 1, small oscillating amplitude at best, at worst errors may make it marginally stable.

b) Function of crystal: behave like an inductor, replace an inductor in an oscillator. inductor over narrow frequency range only.

Advantages: very narrow frequency of operation, precisely defined frequency, low noise, drift, and simple.